



BHARATI VIDYAPEETH'S

INSTITUTE OF COMPUTER APPLICATIONS & MANAGEMENT (BVICAM)

(Affiliated to Guru Gobind Singh Indraprastha University, Approved by AICTE, New Delhi)

A-4, Paschim Vihar, Rohtak Road, New Delhi-110063, Visit us at: <http://www.bvicam.in/>

Course Code: MCA-107

Course Name: Computer Organization

Class Test 1

Time: 1 Hour

Max Marks: 20

Each Question carries 2 marks

1. Digital input signals A,B,C with A as the MSB and C as the LSB are used to realize the Boolean function $f=m_0+m_2+m_3+m_5+m_7$ where m_i denotes the i^{th} minterm. In addition, F has a don't care for m_1 . The simplified expression for F is given by


- (a) $A'C'+B'C+AC$
- (b) $A'+C$
- (c) $C'+A$
- (d) $A'C+BC+AC'$

2. The output expression for K-map shown below is:

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	0	0	1
	11	1	0	1	1
	10	0	0	0	0

- (a) $BD'+BCD$
- (b) $BD'+AB$
- (c) $B'D+ABC$
- (d) $BD'+ABC$

 3. The figure shows a digital circuit constructed using negative edge triggered J-K flip flops. Assume a starting state of $Q_2Q_1Q_0=000$. This state $Q_2Q_1Q_0=000$ will repeat after _____ number of cycles of the clock CLK.



- (a) 5
- (b) 6
- (c) 10
- (d) 7

4. $f(A, B, C, D) = \prod M(0, 1, 3, 4, 5, 7, 9, 11, 12, 13, 14, 15)$ is a maxterm representation of a Boolean function $f(A, B, C, D)$ where A is the MSB and D is the LSB. The equivalent minimized representation of this function is

- (a) $(A+C'+D)(A'+B+D)$
- (b) $AC'D+A'BD$
- (c) $A'CD+AB'CD'+AB'C'D'$
- (d) $(B+C'+D)(A+B'+C'+D)(A'+B+C+D)$

5. Procedure for the design of combinational circuits are:

- A. From the word description of the problem, identify the inputs and outputs and draw a block diagram.
- B. Draw the truth table such that it completely describes the operation of the circuit for different combinations of inputs.
- C. Simplify the switching expression(s) for the output(s).
- D. Implement the simplified expression using logic gates.
- E. Write down the switching expression(s) for the output(s).

- (a) B, C, D, E, A
- (b) A, D, E, B, C
- (c) A, B, E, C, D
- (d) B, A, E, C, D

6. 3 bits full adder contains _____

- (a) 3 combinational inputs
- (b) 4 combinational inputs

- (c) 6 combinational inputs
- (d) 8 combinational inputs

7. How many NOT gates are required for the construction of a 4-to-1 multiplexer?

- (a) 3
- (b) 4
- (c) 2
- (d) 5

8. The characteristic equation of S-R latch is _____

- (a) $Q(n+1) = (S + Q(n))R'$
- (b) $Q(n+1) = SR + Q(n)R$
- (c) $Q(n+1) = S'R + Q(n)R$
- (d) $Q(n+1) = S'R + Q'(n)R$

9. The group of bits 11001 is serially shifted (right-most bit first) into a 5-bit parallel output shift register with an initial state 01110. After three clock pulses, the register contains _____

- (a) 01110
- (b) 00001
- (c) 00101
- (d) 00110

10. A three digit decimal number requires _____ for representation in the conventional BCD format.

- (a) 3 bits
- (b) 6 bits
- (c) 12 bits
- (d) 24 bits